


Q6. Gray Code $\rightarrow$ Binary

a) 01101 (gray)
 $\begin{array}{ccccc} 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 0 & 0 & 1 \end{array}$

b) 10101
 $\begin{array}{ccccc} 1 & 0 & 1 & 0 & 1 \\ 1 & 0 & 1 & 0 & 1 \end{array}$



Assignment - 2 - Boolean Algebra

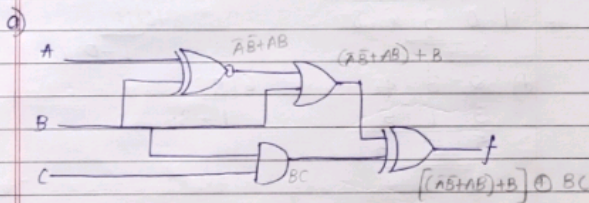1. Derive the output expression 'f' for the below circuits and draw the simplified circuits.




$$\begin{aligned} f &= (\bar{A}B + AB) + B \\ &= \bar{A}B + B(A+1) \\ &= \bar{A}B + B \\ &= \bar{A} + B \end{aligned}$$

$$f = \bar{A} + B$$

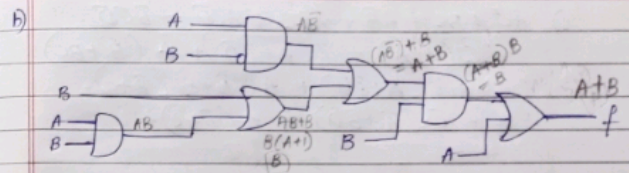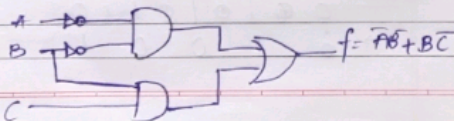

$$f = A + B$$

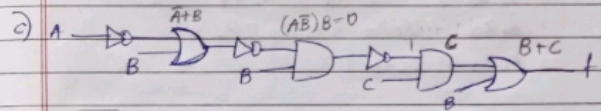

$$\bar{A} + B = A\bar{B}$$

$$f = B + C$$

2. Minimize the Boolean expressions

$$\begin{aligned} a) & \bar{A}CDE + \bar{A}B\bar{D} + ABCE + ABD \\ & \bar{A}D(CE + \bar{B}) + AB(CE + D) \\ & \bar{A}D(\bar{C} + C)(\bar{B} + B) + AB(D + CE) \\ & \bar{A}D(CE + \bar{B}) + AB(D + CE) \end{aligned}$$

$$\begin{aligned} b) & \bar{A}B\bar{C} + ABD + \bar{A}C + \bar{A}C\bar{D} + ACD + A\bar{B}C \\ & = \bar{B}C(\bar{A} + A) + \bar{A}(C + C\bar{D}) + AD(B + C) \\ & = \bar{B}C + \bar{A}C(1 + \bar{D}) + AD(B + C) \\ & = \bar{B}C + \bar{A}C + AD(B + C) \end{aligned}$$

$$\begin{aligned}
 c) & \overline{A}\overline{C} + BC + A\overline{B} + \overline{A}BC + A\overline{C}\overline{D} + \overline{B}C\overline{D} \\
 & BC(1 + \overline{A}) + \overline{C}(\overline{A} + B\overline{D}) + A(\overline{B} + B\overline{C}) \\
 & = BC + \overline{C}(\overline{A} + B\overline{D}) + A(\overline{B} + \overline{C}) \\
 & = BC + \overline{C}(\overline{A} + B\overline{D}) + A(\overline{B} + \overline{C})
 \end{aligned}$$

$$\begin{aligned}
 d) & \overline{x}_1\overline{x}_3\overline{x}_4 + x_3x_4 + \overline{x}_1\overline{x}_2x_4 + x_1x_2\overline{x}_3x_4 + x_2 \\
 & = x_2(x_1\overline{x}_3x_4 + 1) + \overline{x}_1\overline{x}_3\overline{x}_4 + x_3x_4 + \overline{x}_1\overline{x}_2x_4 \\
 & = \overline{x}_1\overline{x}_3\overline{x}_4 + x_3x_4 + \overline{x}_1x_4 + x_2 \\
 & = \overline{x}_1\overline{x}_3 + x_3x_4 + \overline{x}_1x_4 + x_2 \\
 & = \overline{x}_1\overline{x}_3 + x_3x_4 + x_2
 \end{aligned}$$

$$\begin{aligned}
 3. & Z = \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + A\overline{B}C + A\overline{B}C \\
 & Z = A \oplus B \oplus C
 \end{aligned}$$

the entire circuit is equivalent to a 3-input
XNOR gate

4. Minimize the Boolean expressions using K-map.

$$a) f(a,b,c,d) = \sum_m(4,6,8,10,11,12,15) + \sum_d(3,5,7,9)$$

ab \ cd	00	01	11	10
00	0	1	X	3
01	1	X	X	1
11	1		1	
10	1	X	1	1

$$\Rightarrow \overline{a}b + a\overline{b} + a\overline{c}\overline{d} + bcd$$

$$b) f(a,b,c,d) = \pi_m(0,2,4,6,7,9) \cdot \pi_d(10,11)$$

ab \ cd	00	01	11	10
00	0			0
01	0		0	0
11				
10		0	X	X

$$\Rightarrow \overline{a}\overline{d} + \overline{a}b\overline{c} + \overline{a}b\overline{d}$$